

Digital Systems Design and Laboratory

[2. Boolean Algebra]

Chung-Wei Lin

cwlin@csie.ntu.edu.tw

CSIE Department

National Taiwan University

Outline

☒ Introduction

- ☐ Basic Operation
- ☐ Boolean Expressions and Truth Tables
- ☐ Basic Theorems
- ☐ Commutative, Associative, Distributive, and DeMorgan's Laws
- ☐ Simplification Theorems
- ☐ Multiplying Out and Factoring
- ☐ Complementing Boolean Expressions

Introduction

□ Boolean algebra


- Is the basic mathematics for logic design of digital systems

□ History

- George Boole developed Boolean algebra in 1847 and used it to solve problems in mathematical logic
- Claude Shannon first applied Boolean algebra to the design of switching circuits in 1939
 - Master's thesis (21 years old)

□ Switching devices we will use are essentially two-state devices

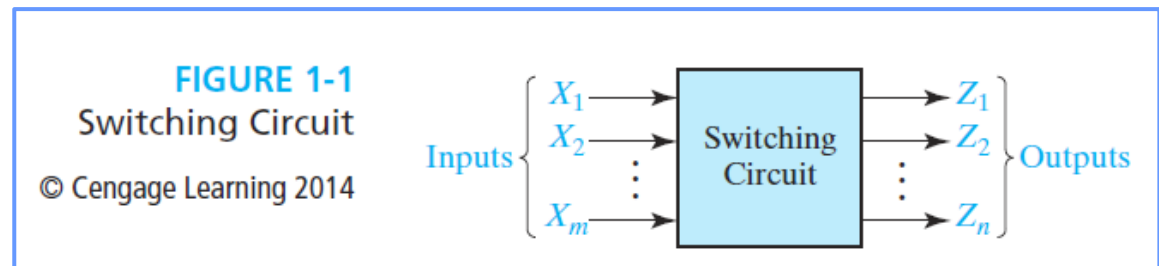- Represent an input or output by a Boolean variable
- 1/0 for High/Low or True/False or Yes/No or Closed/Open
 - Just symbols
 - No numeric value



Outline

☐ Introduction

☒ **Basic Operation**

☐ Boolean Expressions and Truth Tables

☐ Basic Theorems

☐ Commutative, Associative, Distributive, and DeMorgan's Laws

☐ Simplification Theorems

☐ Multiplying Out and Factoring


☐ Complementing Boolean Expressions

Logic NOT

❑ Complement = Inverse = Negate = NOT (' ; $\bar{}$; \sim ; \neg)


➤ $0' = 1, 1' = 0$

➤ Symbol (NOT gate, inverter)

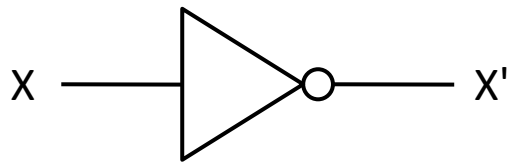

➤ Truth table

X (Input)	X' (Output)
0	1
1	0

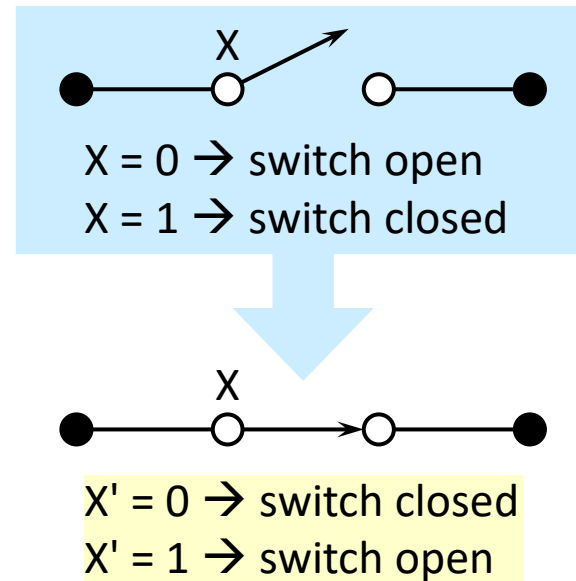


Logic AND

□ AND (\bullet ; \wedge ; sometimes omitted)


➤ $0 \bullet 0 = 0, 0 \bullet 1 = 0, 1 \bullet 0 = 0, 1 \bullet 1 = 1$

➤ Symbol (AND gate)

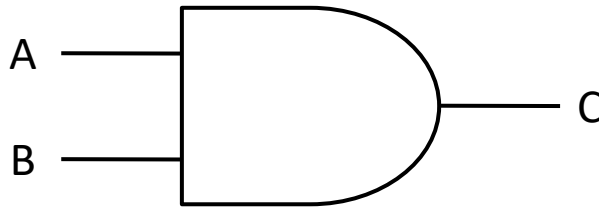

➤ Truth table

A	B	$C = A \bullet B$
0	0	0
0	1	0
1	0	0
1	1	1

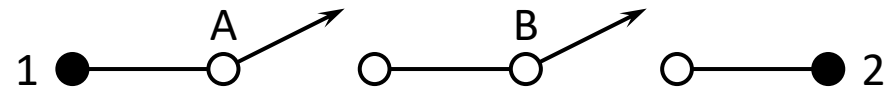

$C = 0 \rightarrow$ open circuit between 1 and 2


$C = 1 \rightarrow$ closed circuit between 1 and 2

Logic OR

□ OR (+ ; ∨)


➤ $0 + 0 = 0, 0 + 1 = 1, 1 + 0 = 1, 1 + 1 = 1$

➤ Symbol (OR gate)

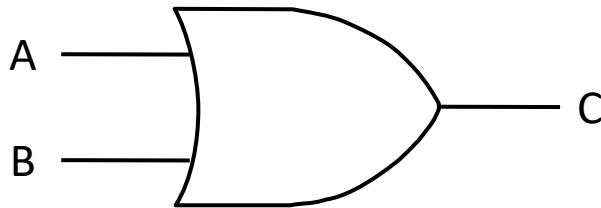

➤ Truth table

A	B	$C = A + B$
0	0	0
0	1	1
1	0	1
1	1	1

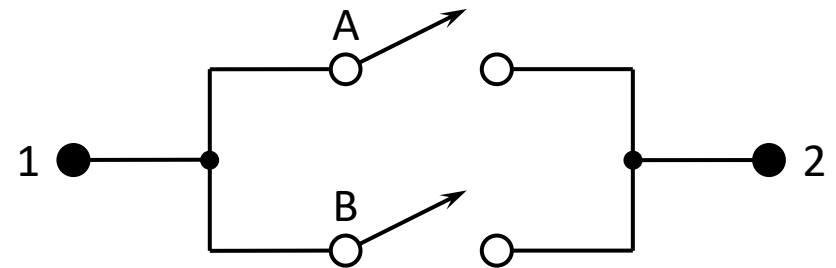

$C = 0 \rightarrow$ open circuit between 1 and 2


$C = 1 \rightarrow$ closed circuit between 1 and 2

Outline


- ☐ Introduction
- ☐ Basic Operation
- ☒ **Boolean Expressions and Truth Tables**
- ☐ Basic Theorems
- ☐ Commutative, Associative, Distributive, and DeMorgan's Laws
- ☐ Simplification Theorems
- ☐ Multiplying Out and Factoring
- ☐ Complementing Boolean Expressions

Boolean Expressions vs. Logic Gates

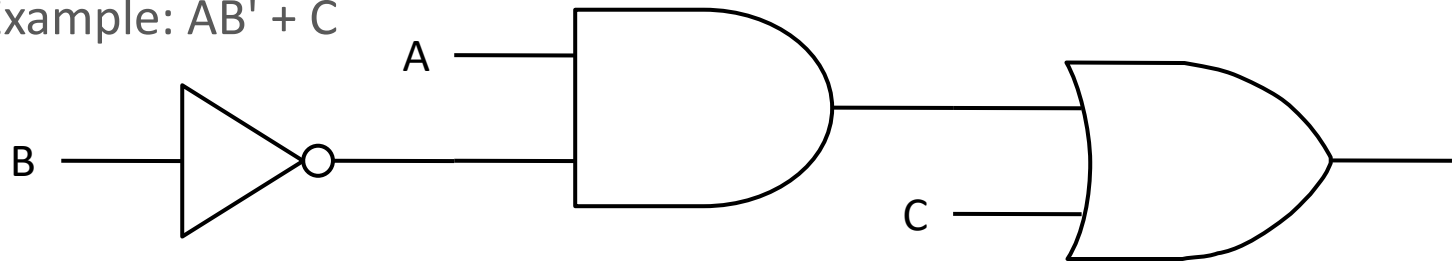- ❑ A Boolean expression is formed by basic operations on constants or variables, e.g., 0, 1, X, Y'
- ❑ Realize a Boolean expression by a circuit of logic gates
 - Perform operations in order: parentheses \rightarrow NOT \rightarrow AND \rightarrow OR
 - Example: $AB' + C$



- Example: $[A(C + D)]' + BE$

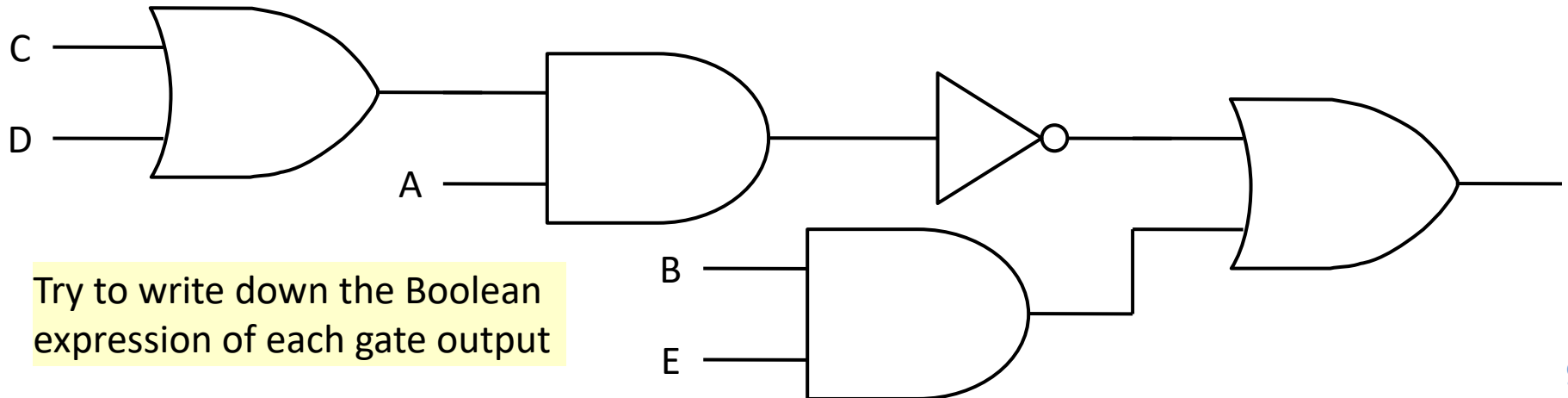

Try to write down the Boolean expression of each gate output

Boolean Expressions vs. Truth Tables

□ A truth table specifies the output values of a Boolean expression for all possible combinations of input values

➤ How to check the equivalence between two expressions?

➤ Example: $AB' + C = (A + C)(B' + C)$

A	B	C	B'	AB'	LHS	A+C	B'+C	RHS
0	0	0	1	0	0	0	1	0
0	0	1	1	0	1	1	1	1
0	1	0	0	0	0	0	0	0
0	1	1	0	0	1	1	1	1
1	0	0	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1
1	1	0	0	0	0	1	0	0
1	1	1	0	0	1	1	1	1

Outline

- ❑ Introduction
- ❑ Basic Operation
- ❑ Boolean Expressions and Truth Tables
- ❑ **Basic Theorems**
 - ❑ Commutative, Associative, Distributive, and DeMorgan's Laws
 - ❑ Simplification Theorems
 - ❑ Multiplying Out and Factoring
 - ❑ Complementing Boolean Expressions

Basic Theorems

□ Operations with 0 and 1

➤ $X + 0 = X$

➤ $X \bullet 1 = X$

➤ $X + 1 = 1$

➤ $X \bullet 0 = 0$

□ Idempotent laws

➤ $X + X = X$

➤ $X \bullet X = X$

□ Involution law

➤ $(X')' = X$

□ Laws of complementarity

➤ $X + X' = 1$

➤ $X \bullet X' = 0$

Outline

- ❑ Introduction
- ❑ Basic Operation
- ❑ Boolean Expressions and Truth Tables
- ❑ Basic Theorems
- ❑ **Commutative, Associative, Distributive, and DeMorgan's Laws**
- ❑ Simplification Theorems
- ❑ Multiplying Out and Factoring
- ❑ Complementing Boolean Expressions

Commutative and Associative Laws

Commutative laws for AND and OR


➤ $XY = YX$

➤ $X + Y = Y + X$

Associative laws for AND and OR

➤ $(XY)Z = X(YZ) = XYZ$

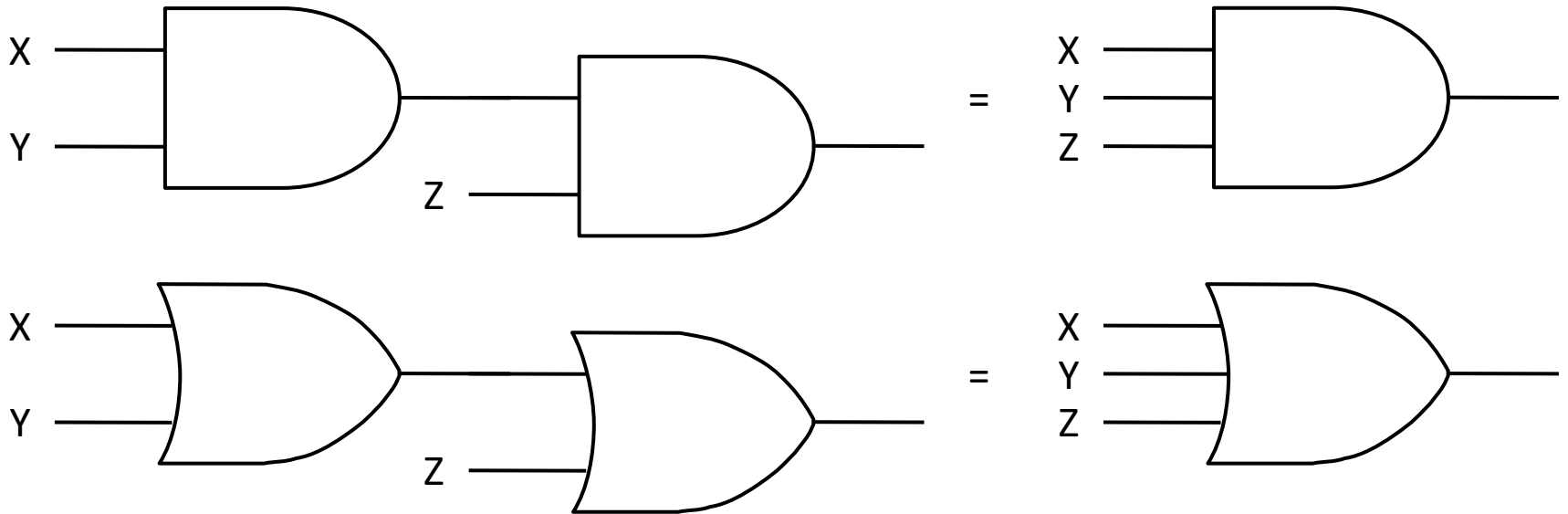➤ $(X + Y) + Z = X + (Y + Z) = X + Y + Z$



Distributive and DeMorgan's Laws

□ Distributive laws

➤ Ordinary one : $X(Y + Z) = XY + XZ$

➤ Second one: $X + YZ = (X + Y)(X + Z)$

- $X + YZ = X \bullet 1 + YZ = X(1 + Y + Z) + YZ = X + XY + XZ + YZ = XX + XY + XZ + YZ$
 $= XX + XZ + YX + YZ = X(X + Z) + Y(X + Z) = (X + Y)(X + Z)$
- You can also use a truth table to prove it

□ DeMorgan's laws

➤ $(X + Y)' = X'Y'$

➤ $(XY)' = X' + Y'$

Duality (1/2)

- ❑ The dual of a Boolean expression is obtained by
 - Interchanging the constants 0 and 1
 - Interchanging the operations of AND and OR
 - Leaving variables and complements unchanged
- ❑ Given a Boolean identity, another identity can be obtained by taking the dual of both sides of the identity

Duality (2/2)

□ Laws of Boolean algebra

- Operations with 0 and 1
 - [1] $X + 0 = X$ [1D] $X \bullet 1 = X$
 - [2] $X + 1 = 1$ [2D] $X \bullet 0 = 0$
- Idempotent laws
 - [3] $X + X = X$ [3D] $X \bullet X = X$
- Involution law
 - [4] $(X')' = X$
- Laws of complementarity
 - [5] $X + X' = 1$ [5D] $X \bullet X' = 0$
- Commutative laws
 - [6] $X + Y = Y + X$ [6D] $XY = YX$
- Associative laws
 - [7] $(X + Y) + Z = X + (Y + Z) = X + Y + Z$
 - [7D] $(XY)Z = X(YZ) = XYZ$
- Distributive laws
 - [8] $X(Y + Z) = XY + XZ$
 - [8D] $X + YZ = (X + Y)(X + Z)$
- DeMorgan's laws
 - [9] $(X + Y)' = X'Y'$
 - [9D] $(XY)' = X' + Y'$

Outline

- ❑ Introduction
- ❑ Basic Operation
- ❑ Boolean Expressions and Truth Tables
- ❑ Basic Theorems
- ❑ Commutative, Associative, Distributive, and DeMorgan's Laws
- ❑ **Simplification Theorems**
- ❑ Multiplying Out and Factoring
- ❑ Complementing Boolean Expressions

Simplification Theorems

□ Uniting

➤ $XY + XY' = X$

➤ $(X + Y)(X + Y') = X$

□ Absorption

➤ $X + XY = X$

➤ $X(X + Y) = X$

□ Elimination

➤ $X + X'Y = X + Y$

➤ $X(X' + Y) = XY$

□ Consensus

➤ $XY + X'Z + YZ = XY + X'Z$

➤ $(X + Y)(X' + Z)(Y + Z) = (X + Y)(X' + Z)$

Simplification Practices

❑ Simplify $Z = A'BC + A'$

❑ Simplify $Z = [A + B'C + D + EF][A + B'C + (D + EF)']$

❑ Simplify $Z = (AB + C)(B'D + C'E') + (AB + C)'$

Outline

- ❑ Introduction
- ❑ Basic Operation
- ❑ Boolean Expressions and Truth Tables
- ❑ Basic Theorems
- ❑ Commutative, Associative, Distributive, and DeMorgan's Laws
- ❑ Simplification Theorems
- ❑ **Multiplying Out and Factoring**
- ❑ Complementing Boolean Expressions

Multiplying Out

❑ Use the distributive laws to multiply out an expression to obtain a sum-of-products (SOP) form

➤ Ordinary distributive law: $X(Y + Z) = XY + XZ$

➤ Second distributive law: $X + YZ = (X + Y)(X + Z)$

❑ Example: multiply out $(A + BC)(A + D + E)$

➤ Use the ordinary distributive law

$$\begin{aligned} \bullet (A + BC)(A + D + E) &= A + AD + AE + ABC + BCD + BCE \\ &= A(1 + D + E + BC) + BCD + BCE \\ &= A + BCD + BCE \end{aligned}$$

➤ Use the second distributive law



$$\bullet (A + BC)(A + D + E) = A + BC(D + E) = A + BCD + BCE$$

SOP vs. Logic Gates

□ Realize SOPs by two-level circuits (AND-OR)

➤ $AB' + CD'E + AC'E'$

➤ $A + B' + C + D'E$

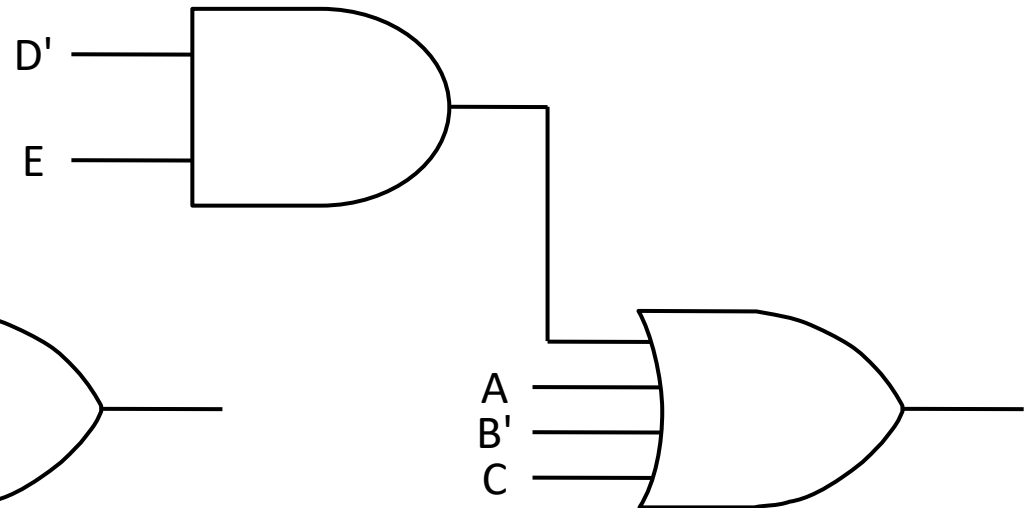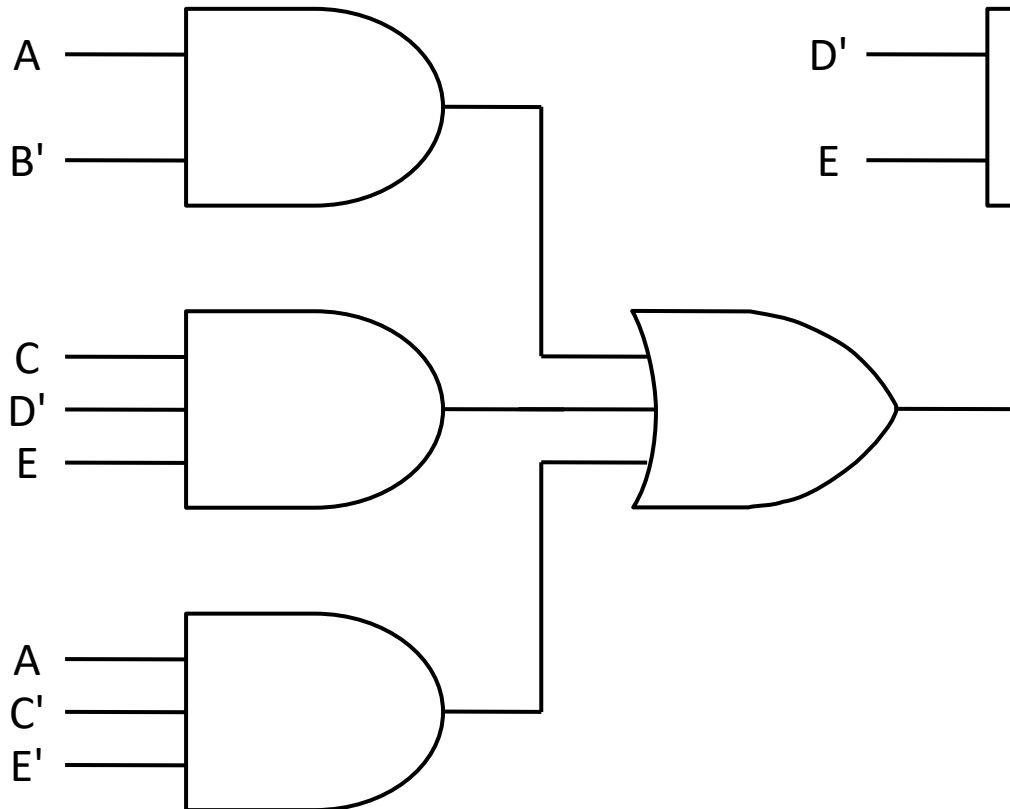

Factoring

- ❑ Use the second distributive law to factor an expression to obtain a **product-of-sums** (POS) form

➤ $\underline{X} + YZ = (X + Y)(X + Z)$

- ❑ Example: factor $A + B'CD$

- ❑ Example: factor $AB' + C'D$



- ❑ Example: factor $C'D + C'E' + G'H$

POS vs. Logic Gates

□ Realize POSs by two-level circuits (OR-AND)

➤ $(A + B')(C + D' + E)(A + C' + E')$

➤ $AB'C(D' + E)$

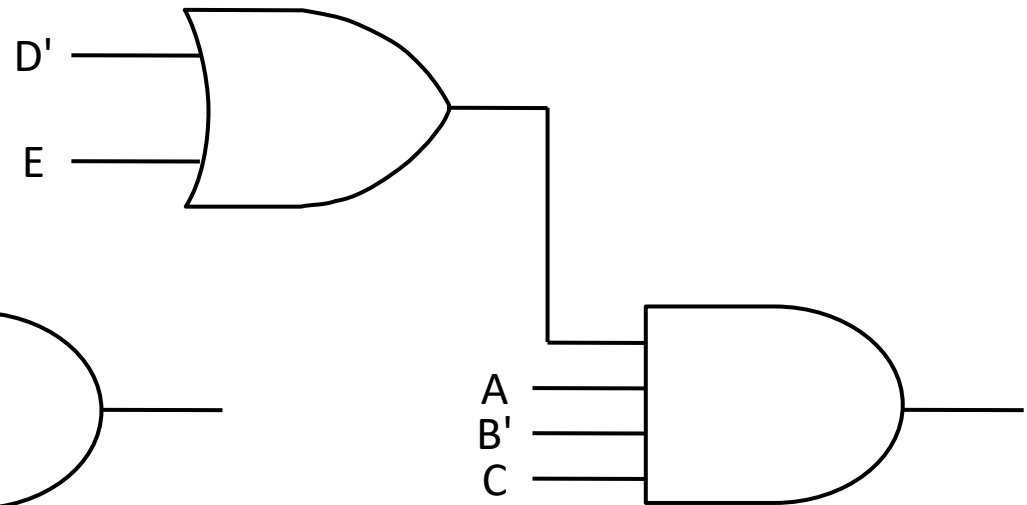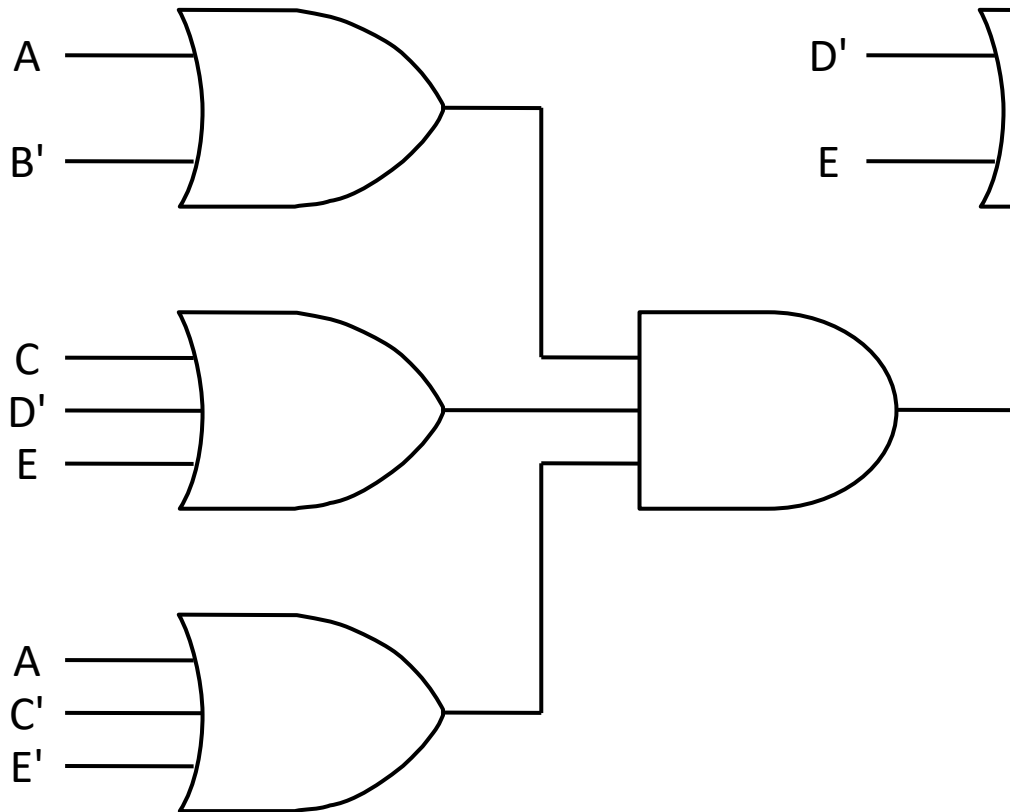

Outline

- ❑ Introduction
- ❑ Basic Operation
- ❑ Boolean Expressions and Truth Tables
- ❑ Basic Theorems
- ❑ Commutative, Associative, Distributive, and DeMorgan's Laws
- ❑ Simplification Theorems
- ❑ Multiplying Out and Factoring
- ❑ **Complementing Boolean Expressions**

Complementing Boolean Expressions

□ DeMorgan's laws with n variables

➤ $(X_1 + X_2 + \dots + X_n)' = X_1' X_2' \dots X_n'$

➤ $(X_1 X_2 \dots X_n)' = X_1' + X_2' + \dots + X_n'$

□ Complement an expression by iteratively applying DeMorgan's laws

➤ Example: complement $(AB' + C)D' + E$ so that NOT is applied only to single variables

- $$\begin{aligned} [(A \bullet B' + C) \bullet D' + E]' &= [(A \bullet B' + C) \bullet D']' \bullet E' \\ &= [(A \bullet B' + C)' + D] \bullet E' \\ &= [(A \bullet B')' \bullet C' + D] \bullet E' \\ &= [(A' + B) \bullet C' + D] \bullet E' \end{aligned}$$

Q&A